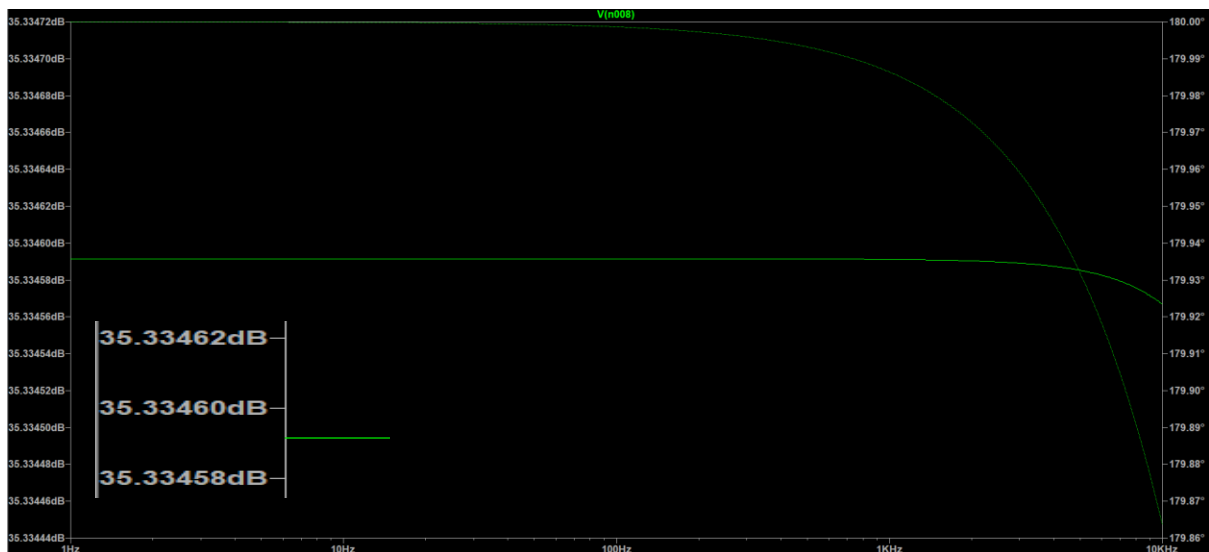


Name: Sarthak Chandra

Entry No: 2020EEB1205

EE301 Analog Circuits – Course Project


180nm




Frequency Response

Gain = 35.3359 dB

Bandwidth = 750kHz

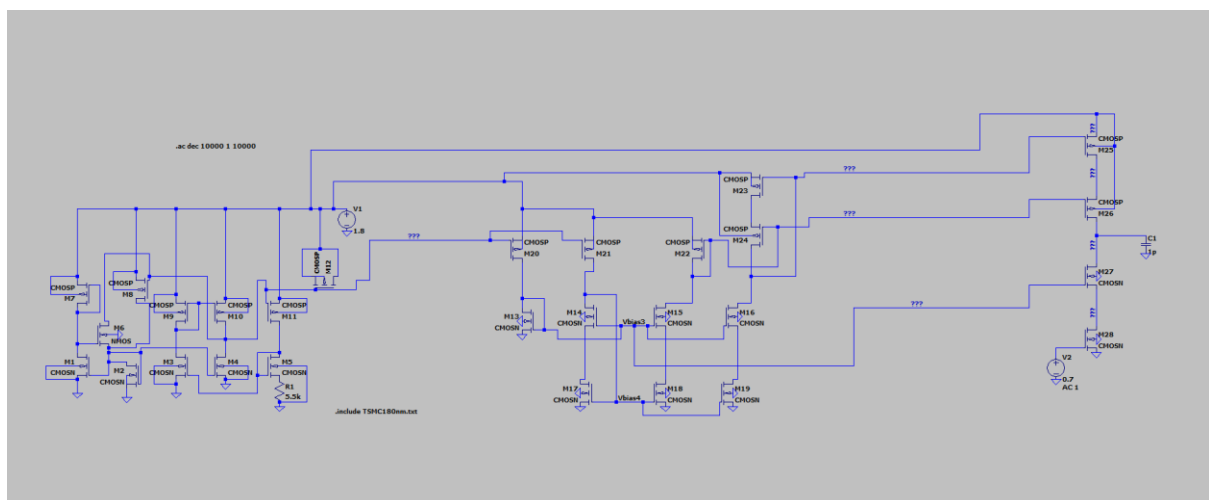


Circuit Diagram for 180nm

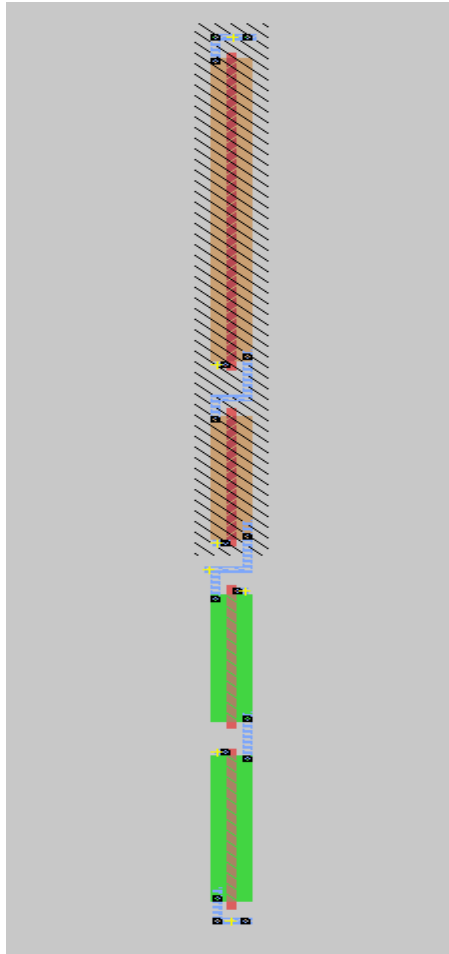

Magic for 180nm


22nm

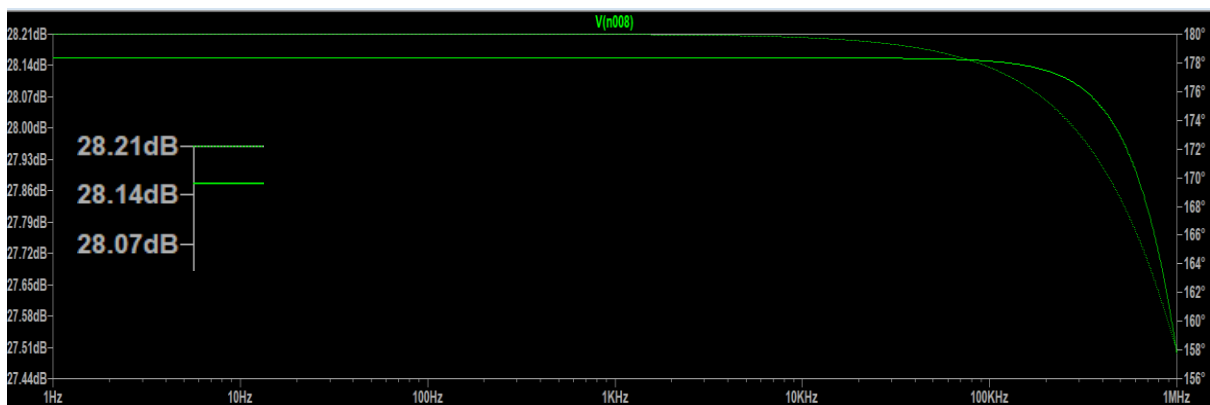

Frequency Response

Gain = 28.15 dB

Bandwidth = 600kHz

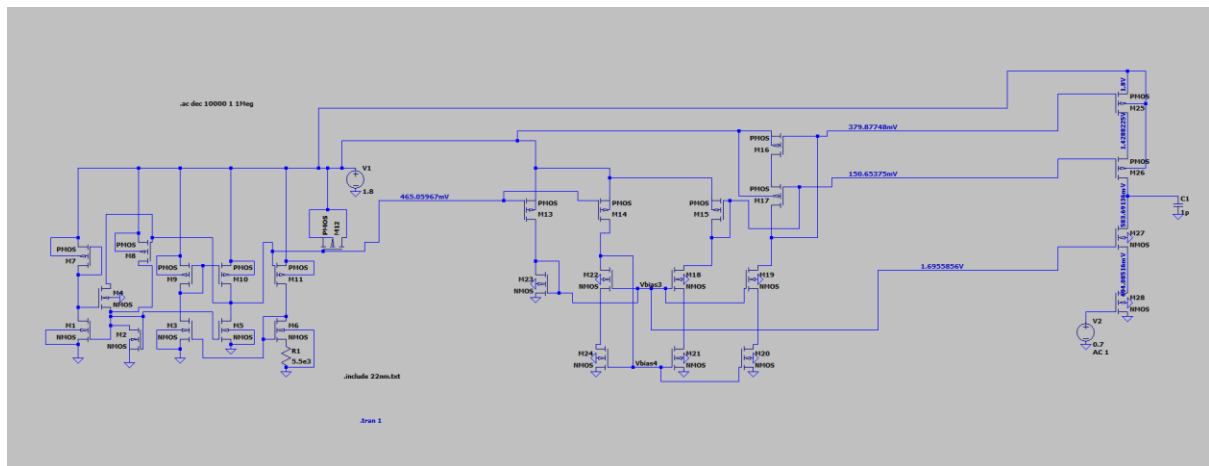

Circuit Diagram for 22nm

Procedure followed for designing 22nm file was the same as that followed for the 180nm File.